

[4]

- d) Determine the input impedance of open and short circuit line.

OR

A lossless RF line has  $Z_0$  of  $600\Omega$  and is connected to a resistive load of  $75\Omega$ . Find the position and length of short circuited stub of same construction as line which would enable the main length of a line to be correctly terminated at 150 mHz.

\*\*\*\*\*

www.rgpvonline.in

www.rgpvonline.in

Total No. of Questions : 5]

[Total No. of Printed Pages :4

Roll No .....

**EC - 505**

**B.E. V Semester**

Examination, December 2015

**Communication Network and Transmission Lines**

*Time : Three Hours*

*Maximum Marks : 70*

- Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.  
ii) All parts of each question are to be attempted at one place.  
iii) All questions carry equal marks, out of which part A and B (Max. 50 words) carry 2 marks, part C (Max. 100 words) carry 3 marks, part D (Max. 400 words) carry 7 marks.  
iv) Except numericals, Derivation, Design and Drawing etc.

### Unit - I

1. a) For symmetrical T network, show that  $\tan h \gamma = \sqrt{\frac{Z_{sc}}{Z_{oc}}}$ .  
b) For symmetrical network define the characteristic impedance.  
c) Design a  $\pi$ -type attenuator with the following specifications. Attenuation = 20 dB, characteristic impedance =  $500\Omega$ .  
d) Determine the image impedance of an asymmetrical L-network.

OR

What is attenuator? Derive design equations for a  $\pi$ -type attenuator.

**Unit - II**

2. a) What are the demerits of m-derived filters?
- b) What is the need of composite filters?
- c) Explain the variations of characteristic impedance ( $z_0$ ), attenuation constant ( $\alpha$ ) and phase constant ( $\beta$ ) with frequency ( $f$ ) with the help of neat sketch in bandpass filters.
- d) Discuss constant - k low pass filter with suitable diagrams. Derive expression for cut-off frequency ( $f_c$ )

OR

Discuss Butterworth approximation for low pass filter.

**Unit - III**

3. a) What is positive real function?
- b) Explain maximum modulus theorem.
- c) Test, whether the polynomial  $s^4 + s^3 + 2s^2 + 3s + 2$  is Hurwitz.
- d) Realize given network in foster I form.

$$z(s) = \frac{2s^2 + s + 1}{s^3 + s^2 + s + 1}$$

OR

Realize the given function in cauer II form

$$z(s) = \frac{2(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$

**Unit - IV**

4. a) What is the difference between lumped parameters and distributed parameters?
- b) Define attenuation constant and phase constant.
- c) What is distortionless line? Derive the condition for distortionless line.
- d) Derive the design equations for full shunt equalizer.

OR

Define input impedance of transmission line. Derive an expression for input impedance of a transmission line in terms of reflection coefficient.

**Unit - V**

www.rgpvonline.in

5. a) Explain standing wave ratio.
- b) What is step matching?
- c) Explain any one method of power measurement on the line.

www.rgpvonline.in