

Total No. of Questions : 10]

[Total No. of Printed Pages : 6

www.rgpvonline.in

Roll No

EC - 305

B.E. III Semester

Examination, December 2012

Network Analysis

Time : Three Hours

Maximum Marks : 70/100

- Note :** 1. Answer Five questions, selecting One question from each unit.
2. All questions carry equal marks.

Unit - I

1. a) Discuss the properties of an ideal current source and an ideal voltage source.
- b) Explain the 'principle of duality'.
- c) Draw the dual of the network shown in Fig. 1

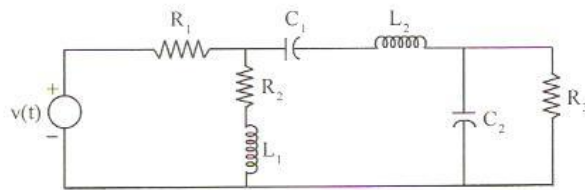


Figure - 1

EC-305

PTO

[2]

OR

2. a) Discuss the properties of series resonant circuits.
 b) In the coupled network of Fig. 2, find the voltage across the 5 ohms resistor. (k – couplin of coefficient)

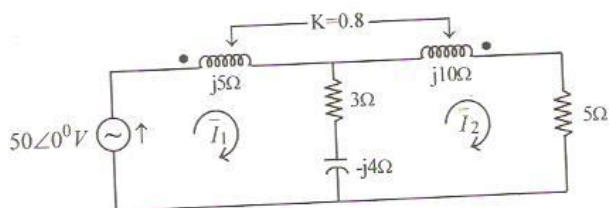


Figure - 2

Unit - II

3. a) Explain the terms, 'tie-set matrix' and 'cut-set matrix' with the help of simple examples.
 b) Using superposition theorem, find the power loss in the 5 ohms resistor of the network of Fig. 3.

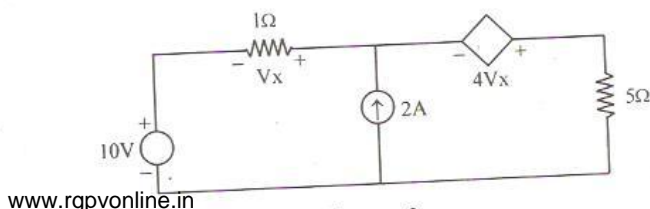


Figure - 3

[3]

OR

4. a) State and explain the following:
- Reciprocity theorem
 - Millman's theorem
- b) Using Thevenin's theorem, find the power in a 1-ohm resistor connected to the terminals A B of the network shown in Fig. 4.

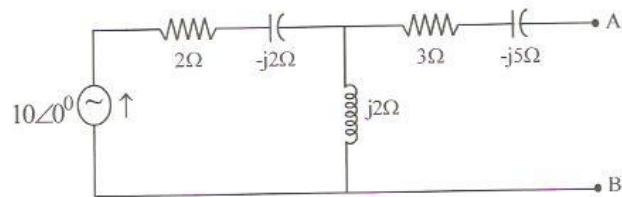


Figure - 4

Unit - III

5. Explain how the initial conditions in networks can be evaluated.

The network of Fig. 5. reaches a steady state with the switch 'k' open. At $t = 0$, the switch 'k' is closed. Find $i(t)$. Sketch the current wave form and indicate the value of the time constant.

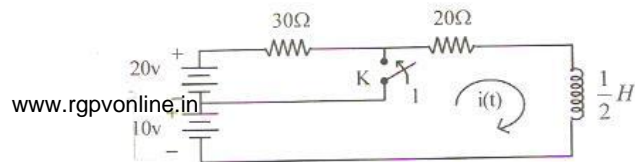


Figure - 5

[4]

www.rgpvonline.in

OR

6. The network of Fig. 6 contains two voltage sources, \bar{v}_1 and \bar{v}_2 . With $\bar{v}_1 = 30 \angle 0^\circ$ V, determine \bar{v}_2 such that the current in $(2 + j3) \Omega$ impedance is zero, using mesh-current method.

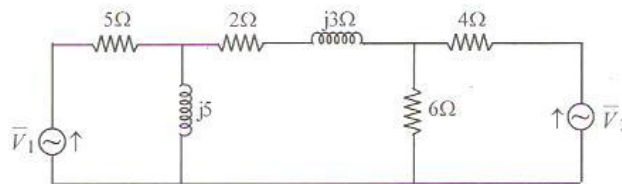


Figure - 6

Unit - IV

7. a) Explain clearly the relationship between impulse, step and ramp functions. Give their standard expressions in time-domain and their laplace transforms.
b) A ramp-voltage $v(t) = r(t - 2)$ is applied to a series R-C network at $t = 0$, when $R = 3 \Omega$ and $C = 1$ F. Assuming zero initial conditions, find $i(t)$.

OR

8. a) What is half-wave symmetry? Explain with the help of an example.
b) Find the trigonometric Fourier series for the wave form shown in Fig. 7 and sketch the spectrum.

www.rgpvonline.in

EC-305

PTO

www.rgpvonline.in

[5]

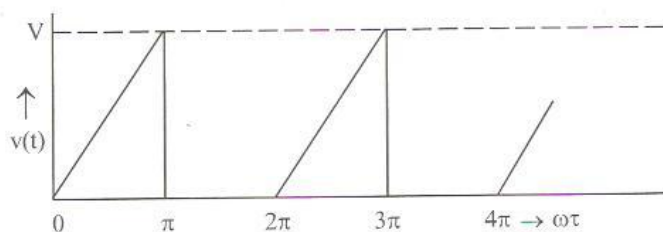


Figure - 7

Unit - V

9. a) Discuss the restrictions on pole and zero locations in s-plane for driving point functions.
- b) Find the open-circuit transfer impedance, $\frac{V_2(s)}{I_1(s)}$ and open-circuit voltage ratio, $\frac{V_2(s)}{V_1(s)}$ for the network shown in Fig. 8.

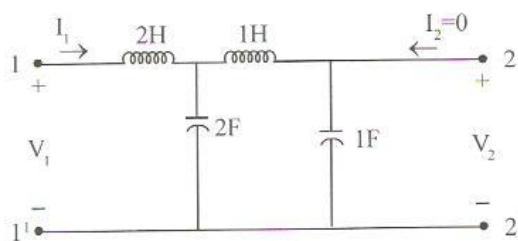


Figure - 8

[6]

OR

10. Define z (open-circuit impedance) parameters of two port networks.

Find the ' z ' parameters of the network shown in Fig. 9.

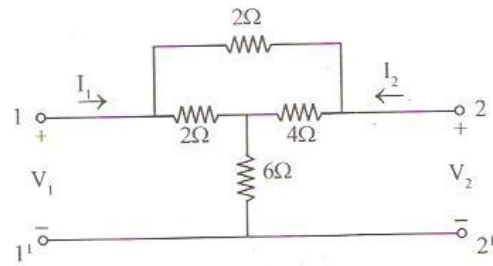


Figure - 9
