

[4]

Write short notes on the following :

- i) PLL
- ii) Fixed and adjustable voltage regulator
- iii) Frequency shift keying

www.rgpvonline.in

Total No. of Questions :5]

[Total No. of Printed Pages : 4

Roll No

EC/EI/IC-404 (New)

B.E. IV Semester

Examination, December 2016

Linear Integrated Circuits and Its Applications

Time : Three Hours

Maximum Marks : 70

- www.rgpvonline.in **Note:** i) Answer five questions. In each question part A, B, C is compulsory and D part has internal choice.
- ii) All parts of each question are to be attempted at one place.
 - iii) All questions carry equal marks, out of which part A and B (Max.50 words) carry 2 marks, part C (Max.100 words) carry 3 marks, part D (Max.400 words) carry 7 marks.
 - iv) Except numericals, Derivation, Design and Drawing etc.

Unit - I

1. a) Draw the block diagram of an Op-Amp and explain it.
- b) Write down the various types and applications of Op-Amp.
- c) Draw the virtual ground of Op-Amp and write down the characteristics of an ideal Op-Amp.
- d) Draw and discuss the inverting and non inverting Op-Amp configurations.

OR

Draw the equivalent circuit of an Op-Amp and write down the expressions for input resistance, voltage gain, collector current and output voltage.

[2]

Unit - II

2. a) Discuss input offset voltage, Input offset current of an Op-Amp.
- b) Discuss input bias current, differential input resistance and input voltage range of Op-Amp.
- c) Discuss common mode rejection ratio and large signal voltage gain of Op-Amp. www.rgpvonline.in
- d) Write short notes on the following :
- i) Slew rate
 - ii) Op-Amp open loop configurations
 - iii) Voltage transfer curve of Op-Amp

OR

Write short notes on the following :

- i) PSRR and gain bandwidth product
- ii) Interpretation of TL082 data sheet

Unit - III

3. a) Discuss the characteristics of positive and negative feedback circuits.
- b) Draw the block diagram of current to voltage converter and show that it is a special case of an inverting amplifier.
- c) Draw the circuit of a summing amplifier and integrators and explain it.
- d) Calculate the voltage gain the input resistance, the output resistance and the bandwidth for a differential amplifier configuration.

www.rgpvonline.in

[3]

OR

Write short notes on the following :

- i) Wien bridge oscillator
- ii) Voltage series and voltage shunt feedback amplifier

Unit - IV

4. a) Give the classification and characteristics of filters.
- b) Discuss low pass filters giving suitable diagram.
- c) Write a short note on notch filter.
- d) Discuss Chebyshev filter and its characteristics giving suitable expressions.

OR

Write short notes on the following :

- i) Butterworth 1st order high pass filter
- ii) All pass filter and self tuned filters

Unit - V

5. a) Write short notes on comparator.
- b) Clipper and clamper circuits.
- c) Discuss zero crossing detector giving suitable diagram.
- d) Draw and discuss monostable multivibrator giving suitable expressions and wave forms.

OR