

Total No. of Questions : 8]

[Total No. of Printed Pages : 2

Roll No

EC-505**B.E. V Semester**

Examination, December 2016

Communication Network and Transmission Lines*Time : Three Hours**Maximum Marks : 70*

- Note:* i) Attempt any five questions out of eight.
 ii) All questions carry equal marks.

1. a) Differentiate between Image impedance and iterative impedance. 7
 b) Discuss characteristics preparation co-efficient and Image transfer co-efficient. 7
2. a) Explain Lattice and Bridged T-networks. 7
 b) Discuss symmetrical and asymmetrical attenuators. 7
3. Discuss passive LC filters. 14
4. Explain LC, RL, RC and RLC network synthesis. 14
5. Explain T and π equivalents of a line. 14

[2]

6. a) Discuss parameters of line and co-axial cable at Radio frequencies. 7
 b) Discuss standing waves. 7
7. Explain the microstrip lines and its analysis. 14
8. Write short notes on any two: 14
 a) Standing wave ratio.
 b) Quarter wave and wave line.
 c) Foster and cauer networks.

www.rgpvonline.in
