

Roll No

EI/IC/CS - 303
B.E. III Semester
Examination, December 2013
Digital Circuit and Systems
Time : Three Hours

Maximum Marks : 70

- Note:** 1. Attempt five questions one from each unit.
2. Assume data wherever necessary.

Unit - I

1. a) Convert : 7
i) $0.1011 \rightarrow$ Decimal
(Binary)
ii) $23_{(8)} \rightarrow$ Decimal
iii) $(9AF)_{(16)} \rightarrow$ Binary
b) State and prove basic laws of Boolean Algebra. 7
OR
2. a) $Y = A\bar{B} + AB$, simplify Boolean equation and the
corresponding logic circuit. 7
b) Prove sum of equation $Y = ABCD + ABC\bar{D}$ using
Karnaugh maps. 7

Unit - II

3. a) Explain the working of Half adder. 7
b) Explain BCD adders. 7

EI/IC/CS-303

www.rgpvonline.in

PTO

[2]

OR

4. a) Explain Half subtractor circuit. 7
b) Explain Full Adder. 7

Unit - III

5. a) Explain Astable multivibrator. 7
b) Explain working of PMOS, NMOS and CMOS logic. 7

OR

6. a) Explain Linear waveshaping circuits. 7
b) Explain Schmitt Trigger. 7

Unit - IV

7. a) Explain Multiplexers and Demultiplexers. 7
b) Explain counters. 7

OR

8. a) Explain the working of encoders. 7
b) Explain PLA's. 7

Unit - V

9. What is the resolution of a 9 bit D/A converter which uses a ladder network? What is this resolution expressed as a percent? If the full scale output voltage of this converter is +5V, what is the resolution in volts. 14

OR

10. a) Explain AID converter and its working. 7
b) State maximum conversion time and average conversion time. 7
