

6. Determine the Fourier series expression of the waveform shown in figure 10.

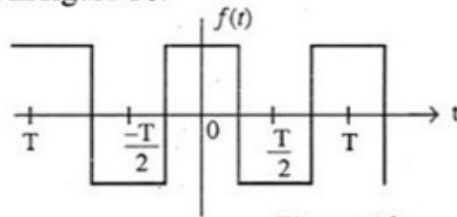


Figure 10

7. a) Determine the Z-parameters for the network shown in figure 11.

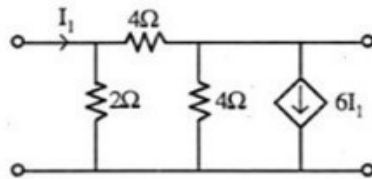


Figure 11

- b) Determine the Y-parameters of the network shown in figure 12.

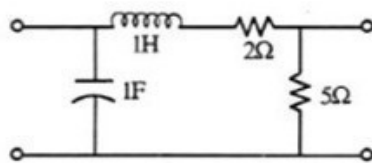


Figure 12

8. Write short notes on any two of the following :
- Series and parallel resonance
 - Tie set schedule
 - Hybrid parameters

EC-305**B.E. III Semester**

Examination, December 2016

Network Analysis

Time : Three Hours

Maximum Marks : 70

- Note: i) Attempt any five questions.
ii) All questions carry equal marks.

1. a) Draw the dual network of following circuit figure 1.

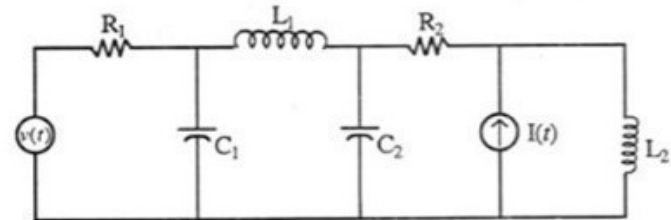


Figure 1

- b) Write the loop equations of magnetically coupled circuit shown in figure 2.

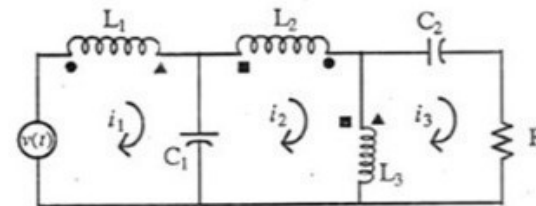


Figure 2

2. a) By superposition theorem calculate current I in the circuit shown in figure 3.

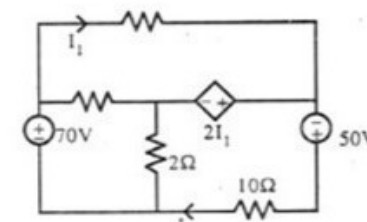


Figure 3

- b) Find the Norton equivalent circuit across the terminal AB of the circuit shown in figure 4.

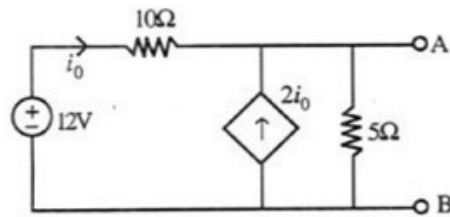


Figure 4

3. a) Calculate the current in the 6Ω resistor of the circuit shown in figure 5 using Thevenine theorem.

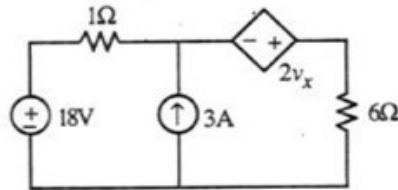


Figure 5

- b) State and prove maximum power transfer theorem.
4. a) In the circuit shown in figure 6 the switch S is closed at $t = 0$ connecting a source e^{-t} to the RC circuit. At $t = 0$, it is observed that the capacitor voltage has the value $v_c(0) = 0.5V$. Determine $v_2(t)$.

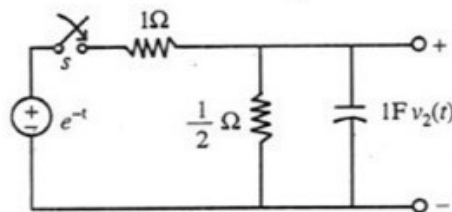


Figure 6

- b) In the circuit of figure 7, after the switch has been in the open position for a long time, it is closed at $t = 0$. Find the voltage across the capacitor.

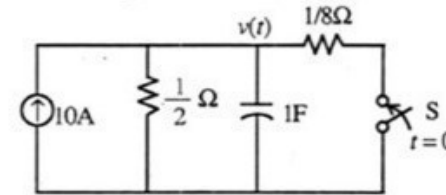


Figure 7

- a) In the circuit of figure 8 at time t_0 after the switch S was closed, it is found that $v_2 = +5V$. It is required to determine the value of $i_2(t_0)$ and $\frac{di_2(t_0)}{dt}$.

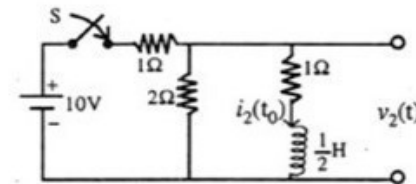


Figure 8

- b) In the circuit of figure 9 the switch S is in position 'a' for a long time. At $t = 0$ the switch is moved from 'a' to 'b'. Find $v_2(t)$ using numerical values given in the circuit. Assume that the initial current in $2H$ inductor is zero.

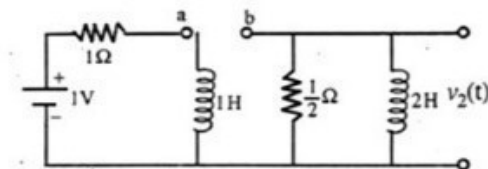


Figure 9