

Roll No

EC - 8012**B.E. VIII Semeste**

Examination, June 2015

Microwave Circuits**Elective - II****Time : Three Hours**www.rgpvonline.in **Maximum Marks : 70**

- Note:** i) Attempt any one question from each unit.
 ii) All question carry equal marks.
 iii) Assume suitable data if any missing.

UNIT-I

1. a) What is the significance of impedance matching? Explain impedance match factor in brief. 7
 b) Explain (i) single stub matching (ii) Double stub matching. Enumerate the advantages and disadvantages of each of these methods. 7

OR

2. a) Write a detail note on Binomial transformer. 7
 b) A typical transmission line has a resistance of $8\Omega/Km$ impedance of $2\text{ m}\Omega/km$, a capacitance of $0.002\text{ }\mu F/\mu m$ and a conductance of $0.07\text{ }\mu S/km$. Calculate the characteristic impedance, attenuation constant, phase constant of transmission line at a frequency of 2 kHz . If a signal 82 volt is applied and the line is terminated by its characteristic impedance, calculate the power delivered to the load, if the length of line is 500 km . 7

UNIT-II

3. a) What are the different substrates available for microwave printed circuits? Explain in detail. 7
 b) Discuss various types of losses in microstrip lines and also define Quality factor of microstrip line. 7

EC-8012

PTO

[2]

OR

4. a) What do you understand by co-planer strip lines? 7
 b) A lossless parallel strip line has a conducting strip width W . The substrate dielectric separating the two strips has relative dielectric constant ϵ_{rd} of 6 and thickness d of 4 mm . Calculate, width W of strip in order to have characteristic impedance of 50Ω , strip line capacitance, strip line inductance and phase velocity of the wave in parallel strip. 7

UNIT-III

5. a) Discuss design procedure of low noise Amplifier. 7
 b) Explain microwave amplifier design using 'S' parameters. 7

OR

6. Explain in detail: 14
 a) Power gains
 b) Stability

UNIT-IV

7. Explain the following: 14
 a) Gunn oscillator
 b) Balanced mixer

OR

8. a) What do you understand by Oscillators phase noise? 7
 b) Explain mixer analysis using Harmonic Balancing. 7

UNIT-V

9. a) Explain the implementation of stepped impedance low pass filter. 7
 b) What do you understand by frequency transformation and expansion? 7

OR

10. a) Write a note on Narrowband and Wideband microwave filter. 7
 b) Discuss image parameter method of filter design in brief. 7